

S.S.P.Mandal Tehu's

**Rani Laxmibai Mahavidyalaya Parola**

**Parola (Dist-Jalgaon)**

NAAC Accredited 'B' Grade



## CERTIFICATE

Student's Name Nikam Harshal Aadhar

Std T.Y.BSC.

Class T.Y.BSC. Division \_\_\_\_\_

This is to certify that experiment's written in the index has been performed by the student satisfactorily.

Internal Examiner

Teacher's Signature

External Examiner

Head of the Department





S.S.P.Mandal Tehu's

# Rani Laxmibai Mahavidyalaya Parola

## Department of Physics

Name: Nikam Harshal Aadhar Lab. No. \_\_\_\_\_


Batch \_\_\_\_\_ Date 1 / 1 / 2022 Expt. No. 1

Title Astable multivibrator using IC-555


Aim :- TO determine build and tests on astable multi-vibrator using IC-555

App :- IC-555, resistor, capacitor, CRO, 5v dc, power supply, etc.

Fig :-

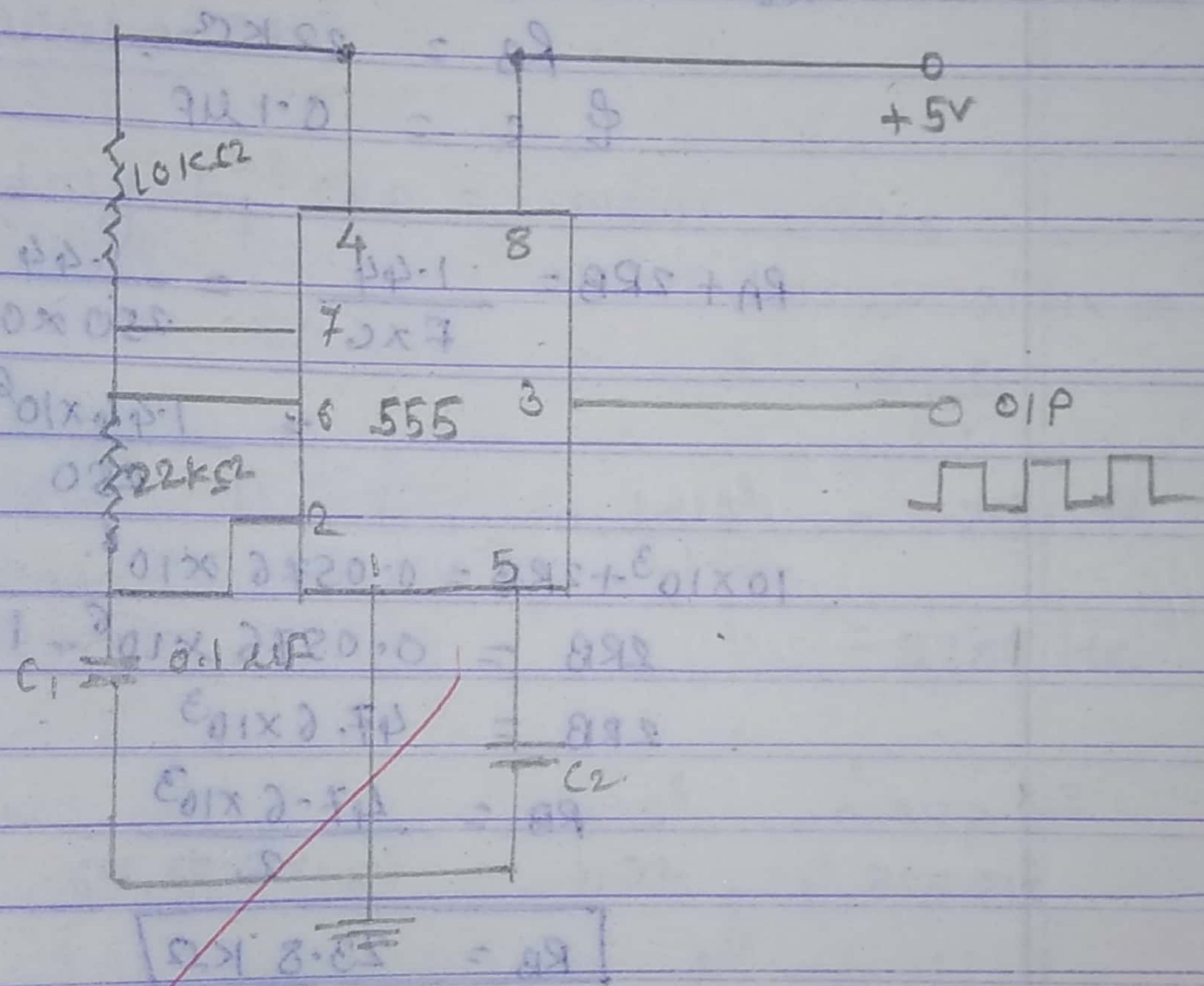

Observations :-

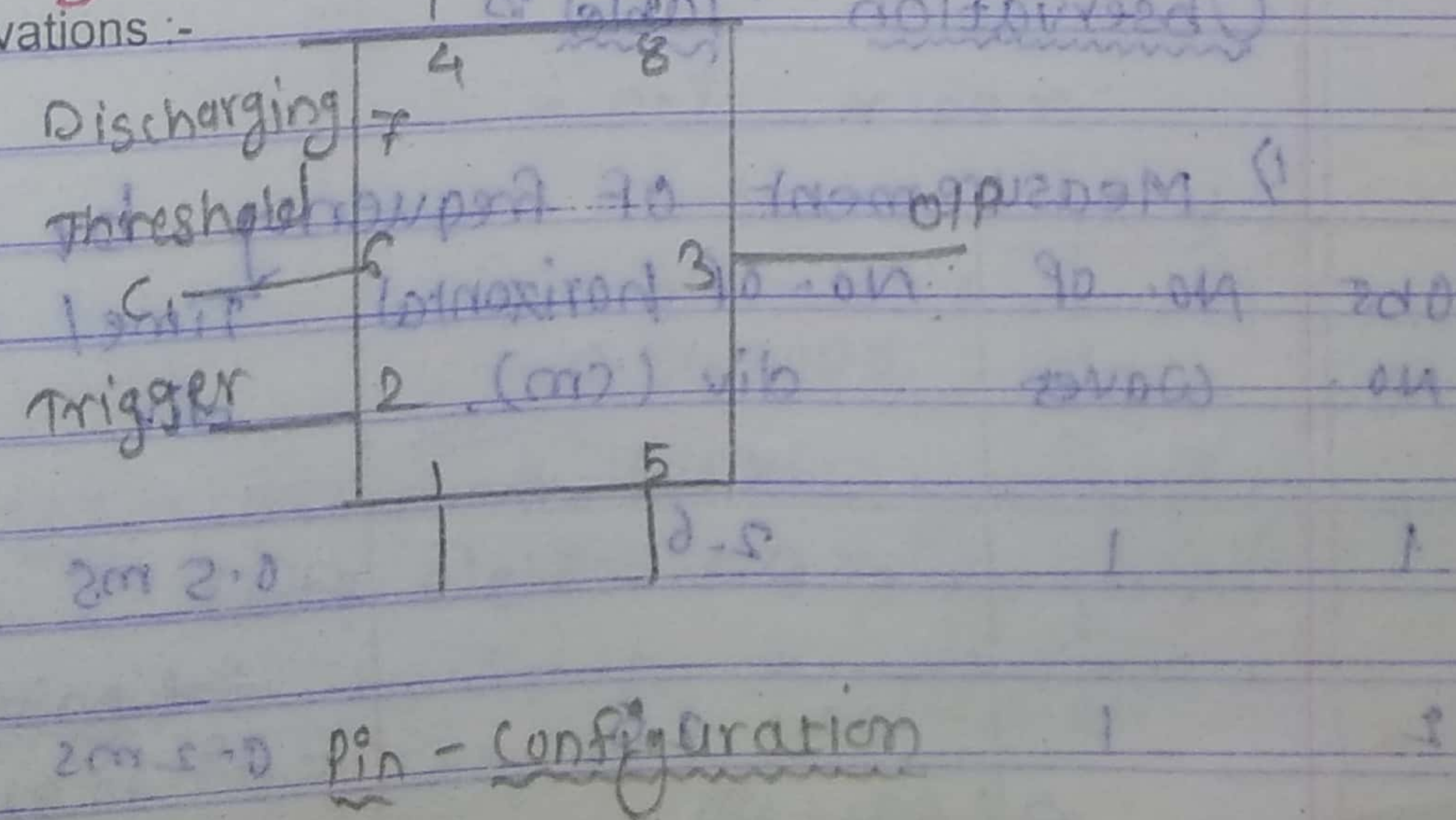

complete for  
 observation  
 calculation  
 graph  
 figure  
 procedure  
 general

pin - configuration

## Designing :-

Design the astable multivibrator for frequency 250 Hz.

The frequency of astable multivibrator

$$f = \frac{1.44}{(R_A + 2R_B) \cdot C}$$

Given =  $f = 250 \text{ Hz}$ .

assume,  $C = 0.1 \mu\text{F} = 0.1 \times 10^{-6} \text{ F}$ .

Let  $R_A = 10 \times 10^3 \Omega$

$$R_B = 22 \text{ k}\Omega$$

$$C = 0.1 \mu\text{F}$$

$$R_A + 2R_B = \frac{1.44}{f \times C} = \frac{1.44}{250 \times 0.1 \times 10^{-6}}$$
$$= \frac{1.44 \times 10^6}{250}$$

$$10 \times 10^3 + 2R_B = 0.0576 \times 10^6$$

$$2R_B = 0.0576 \times 10^6 - 10^3 \times 10$$

$$2R_B = 47.6 \times 10^3$$

$$R_B = \frac{47.6 \times 10^3}{2}$$

$$R_B = 23.8 \text{ k}\Omega$$

## Observation Table :-

1) Measurement of frequency by CRO :-

Obs No.	No. of waves	No. of horizontal div (cm).	Time/div	Frequency (Hz)
1	1	2.6	0.5 ms	769
2	1	2.6	0.2 ms	757

2) Duty cycle by CRO.

1) No. of div frequency for $T_{ON} = 1.4$	Time / Div = 0.5 ms	$T_{ON} = 0.7 \times 10^3$ = 0.7 ms.
2) No. of div = 2.6	Time / Div = 0.5 ms	$T = 1.3$ ms.

Duty cycle is = 54 %

### # Calculation

1) Frequency by CRO =  $\frac{\text{No. of waves}}{\text{No. of horizontal div} \times \frac{\text{time}}{\text{Div}}}$

$$f = \frac{1}{2.6 \times 0.5 \times 10^{-3}} = \frac{1 \times 10^3}{1.32} = 0.759 \times 10^3 = 759 \text{ Hz.}$$

$$f = \frac{1}{6.6 \times 0.2 \times 10^{-3}} = \frac{1 \times 10^3}{1.32} = 0.75 \times 10^3 = 757 \text{ Hz.}$$

2) Duty cycle by CRO =  $\frac{T_{ON}}{T} \times 100\%$

$$= \frac{0.7}{1.3} \times 100\%$$

$$= 0.54 \times 100$$

Duty cycle = 54 %

### Designing

1) Value of  $R_B = \text{Let } f = \frac{1.44}{(R_A + 2R_B) \cdot C}$

consider  $R_A = 1\text{K}\Omega$ ,  $C = 0.01\ \mu\text{F}$ ,  $F = 710\ \text{Hz}$ .

$$1 \times 10^3 = \frac{1.44}{(1 \times 10^3 + 2R_B) \times 0.01 \times 10^{-6}}$$

By solving above equation for  $R_B$ ,  
get  $R_B = 100\ \text{k}\Omega$

Required value of  $R_B$  to connecting  
circuit  $R_B = 100\ \Omega$

1) Duty cycle :-

$$\text{Let } D = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

$$= \frac{1 \times 10^3 + 100 \times 10^3}{(1 \times 10^3) + 2 \times 100 \times 10^3} \times 100\%$$

$$= \frac{101 \times 10^3}{1 + 200 \times 10^3} \times 100\% = \frac{101}{201} \times 100\%$$

$$= 0.0049 \times 100\% = 49\%$$

$$D = 0.5 = 50\%$$

Theory :- An astable multivibrator is called for running multivibrator is a rectangular wave generating circuit unlike the monostable multivibrator. This ckt does not require any external trigger to change the state of O/P. Hence the name free running. An astable multivibrator can be produced by adding resistance & a capacitor to the base of timer IC as illustrated in fig. The timing during which the output is either high or low is determined by externally connected resistor & capacitor.

# Results :-

1) Designed value for frequency of astable multivibrator = 100 Hz

2) Frequency obtained from CRO = 769 Hz

3) Duty cycle from circuit value = 50%

4) Duty cycle as obtained from CRO = 54%

*(Signature)*

# Rani Laxmibai Mahavidyalaya Parola

## Department of Physics

Name: Nikam Harshal Aadhar Lab. No. \_\_\_\_\_

Batch \_\_\_\_\_ Date \_\_\_\_/\_\_\_\_/20\_\_\_\_ Expt. No. 2


Title Specific heat of Graphite

Aim :-

To determine the specific heat of graphite at different temperature.

App :- specific heat kit, diameter, voltmeter, ammeter, thermometer, etc

Fig :-

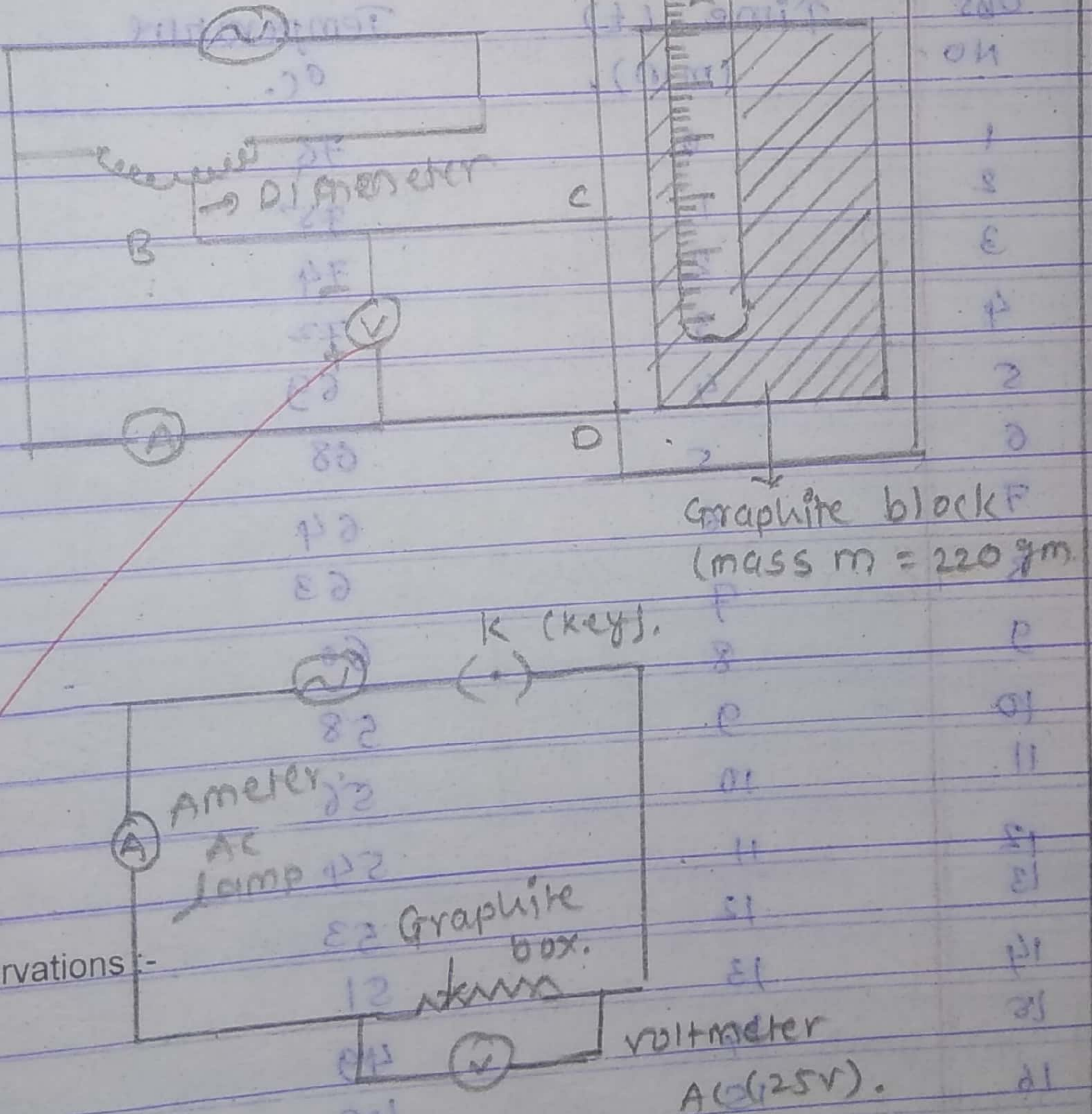

Observations :-

Observations :-

- i) Mass of graphite block (M) = 220 gm
- ii) Joule's Constant  $J = \underline{\underline{4.2 \text{ Joules}}}$

complete for

Observation

Calculation

Graph

Figure

Procedure

General

# Observation Table :-

Obs No	Current I (mA)	Voltage V (volt)	Equilibrium temp °C	Power
1)	$I_1 = 0.53$	$V_1 = 15V$	$80^\circ$	$7.95$
2)	$I_2 = 0.68$	$V_2 = 17V$	$70^\circ$	$11.56$

$V = 20V$  &  $I = 0.7A$

Obs No	Time (t) (min)	Temperature °C
1	0	78
2	1	75
3	2	74
4	3	72
5	4	69
6	5	68
7	6	64
8	7	63
9	8	60
10	9	58
11	10	56
12	11	54
13	12	53
14	13	51
15	14	49
16	15	48

(ii) Joule's Constant  $J = \frac{W}{Joule}$


Mass of propyne (M) = 200 gm

Observations :-



## # Experimental Procedure

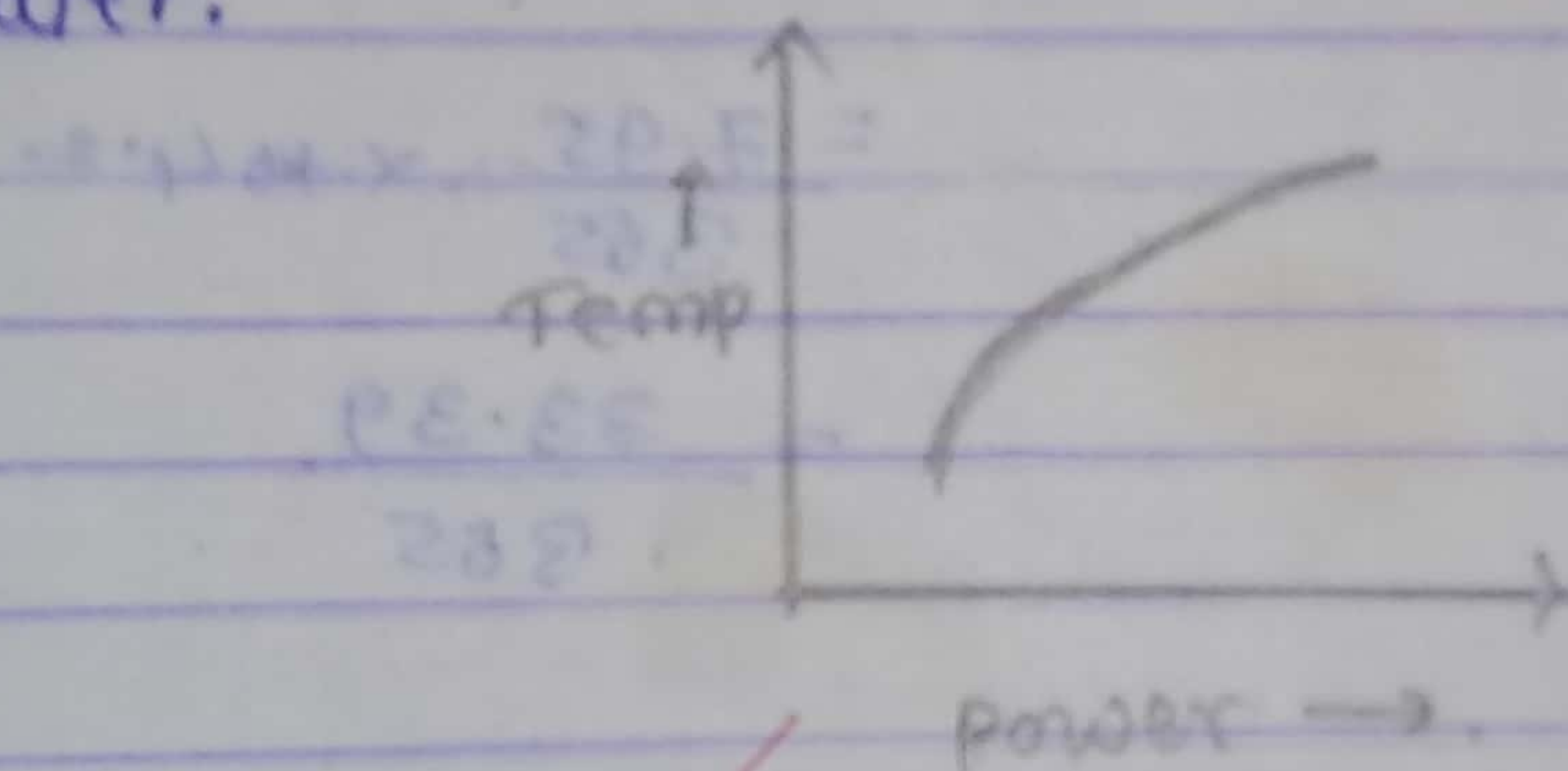- 1) connect the circuit as shown in fig. with paper ammeter galvanometer.
- 2) Power supply value to the later 25V with the help of diastanorstand as a unit an equilibrium dipole attained, The note down value of current temp. with help of thermometer.
- 3) Now increases the voltage of dimeter state from 20% to 25 volt obtained required equilibrium temperature circuit. This voltage is note down, the gives voltage and current in the circuit for graph shows equilibrium. Obtain corresponding to power supplies to the heater.



4) Similarly, Note down the equation of equilibrium for heater voltage varies in steps

5) About six eq<sup>n</sup> temp of tabular data

shown in Fig in table ①

⑥ Provide the heater will fullfill power i.e. zero volt allows the block the heat unit equation temperature is released. This temp will be granual 50.00°C switch off heater.

⑦ Plot the graph between specific heat is the temperature graph shows variation of specific heat.

Temp to temp specific heat

Temp to temp specific heat

# Calculation

Formula:

$$P = VI$$

$$\text{specific heat } = S = \frac{VI}{m(\text{slope})\theta}$$

i)  $P_1 = V_1 I_1 = 15 \times 0.53 = 7.95 \text{ kcal}$

ii)  $P_2 = V_2 I_2 = 17 \times 0.08 = 1.50 \text{ kcal}$

iii)  $S_1 = \frac{V_1 I_1}{m(\text{slope})\theta}$

$$= \frac{15 \times 0.53}{220 \times (1.66)} \times 4.2$$

$$= \frac{7.95 \times 4.2}{365}$$

$$= \frac{7.95}{365} \times 4.2$$

$$= \frac{33.39}{365}$$

$$S_1 = 0.314 \text{ cal/gm}^\circ\text{C}$$

$$S_2 = \frac{V_2 I_2}{m(\text{slope})\theta}$$

$$= \frac{17 \times 0.68}{220 \times 2.8} \times 4.2 = \frac{11.50 \times 4.2}{550}$$

$$= \frac{48.55}{550}$$

$$S_2 = 0.0882 \text{ cal/gm}^\circ\text{C}$$

$$S = \frac{S_1 + S_2}{2} = \frac{0.314 + 0.0882}{2} = 0.2011$$

$$S = 0.0898$$

\* Result: The specific heat of graphite

$$S = 0.0898 \text{ cal/gm}^\circ\text{C}$$

Name :- Nikam Harshal Aadhar Std :- \_\_\_\_\_

Date :- \_\_\_\_\_

Specific heat of Graphite.

Scale - x-axis = 1 cm = 1 min

Y-axis = 1 cm = 2°C


i) slope =  $\frac{d\theta}{dt} = \frac{72-68}{5-3} = \frac{4}{2}$

Slope = 2

ii) Slope  $\frac{d\theta}{dt} = \frac{53-49}{14-12} = \frac{4}{2} = \frac{4}{2}$

Slope = 2

Temperature →

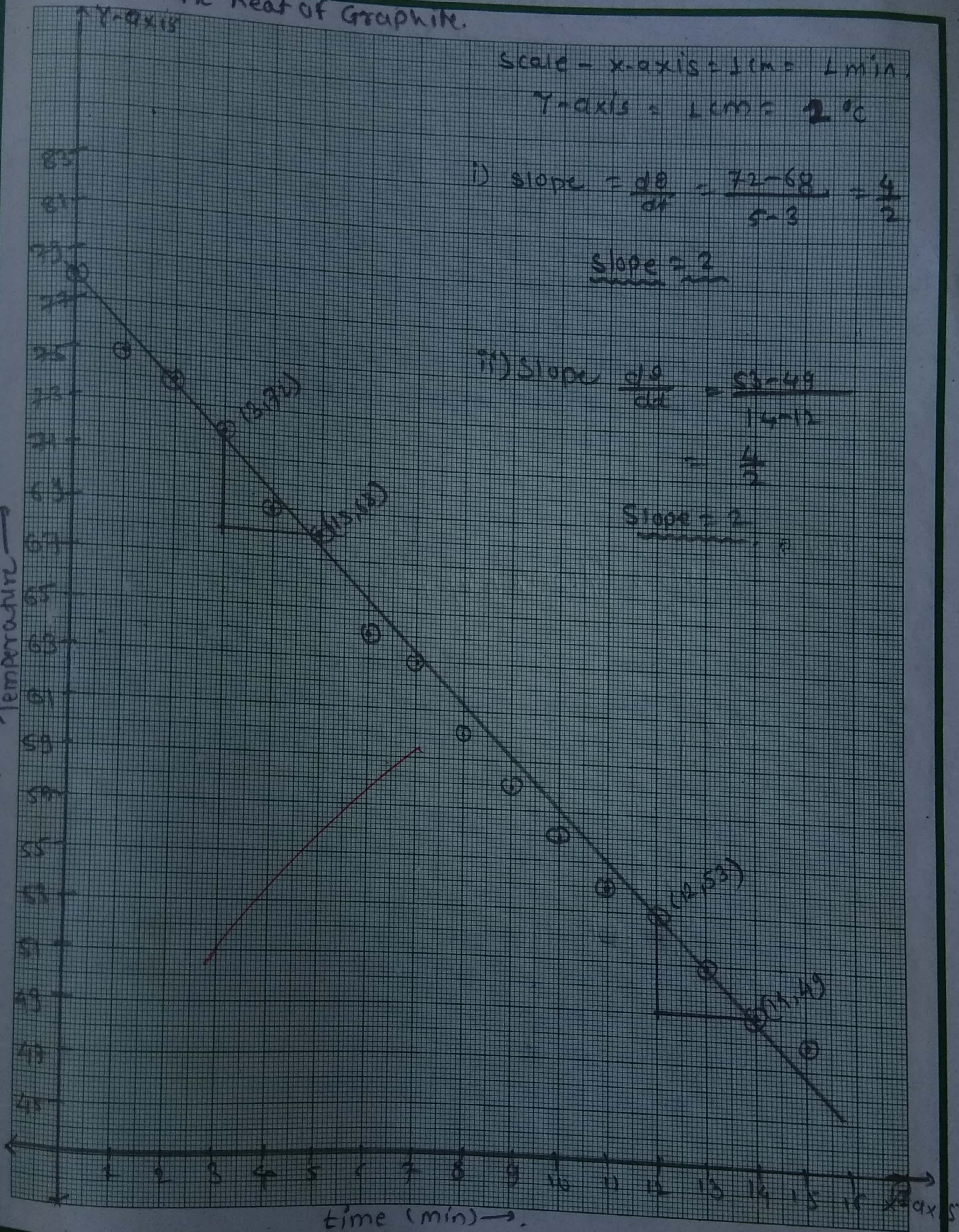

Scale: